

(i) Printed Pages: 3 Roll No. ....

(ii) Questions : 7 Sub. Code : 

0	5	4	5
---	---	---	---

Exam. Code : 

0	0	0	6
---	---	---	---

**B.A./B.Sc. (General) 6<sup>th</sup> Semester**

**1059**

**PHYSICS**

**Paper—B : Electronics and Solid State Devices—II**

**Time Allowed : Three Hours] [Maximum Marks : 22**

**Note :—** (1) Attempt *five* questions in all, selecting *two* from each Unit I and II. Unit III (question no. 7) is compulsory.

(2) Use of non programmable calculator is allowed.

**UNIT—I**

1. (a) Draw the structure and characteristics of p-channel depletion MOSFET. Discuss its working. 3
- (b) Common source FET amplifier has a load resistance of 500 k $\Omega$ . If the a.c drain resistance and amplification factor are 100 k $\Omega$  and 0.15 mA/V respectively, calculate the voltage gain of the amplifier. 1½
2. (a) Explain, with the help of a block diagram, the working principle of a feedback amplifier. Find the expression for the voltage gain with feedback. 3
- (b) State Barkhausen Criterion for sustained oscillations. Give an expression for the frequency of oscillation and condition for the sustained oscillation. 1½

3. (a) Draw the circuit diagram of Wein Bridge Oscillator. Explain the principle of its operation. Show that the amplifier used in it must have again greater than 3 for sustained oscillations. 3
- (b) A MHz Colpitt's oscillator is generating waveforms of frequency 16 MHz. The coil used in it has inductance of 10 mH and transistor has  $h_{fe} = 50$  and  $\Delta_{he} = 0.5$ . Find the value of the capacitance.  $1\frac{1}{2}$

## UNIT—II

4. (a) Write the characteristics of an ideal operational amplifier. Discuss its application as differentiator. 2
- (b) Explain the working of astable multivibrator using IC555 Timer. Also, derive an expression for frequency and duty cycle of multivibrator.  $2\frac{1}{2}$
5. (a) What is the need for modulation ? Derive an expression for amplitude modulated wave with sinusoidal modulation.  $2\frac{1}{2}$
- (b) Write a short note on skip distance and selective fading. 2
6. (a) What do you understand by standard form of SOP ? Explain with example the method to convert SOP expression into canonical SOP form. 2
- (b) Solve the following Boolean expression and draw the simplified logic circuit and its truth table :  $\overline{A}\overline{B}\overline{C} + \overline{A}B\overline{C} + A\overline{B}\overline{C} + ABC$   $1\frac{1}{2}$
- (c) State De Morgan's theorem. 1

### UNIT—III

#### (Compulsory Question)

7. Attempt any *eight* questions :
- (a) Why is NAND gate considered as the building block of digital electronics ?
  - (b) Convert the following binary number  $(1100.1011)_2$  to decimal number.
  - (c) What are the applications of emitter follower ?
  - (d) Why OP-Amp is generally not used in open loop mode ?
  - (e) Name the various modes of propagation of radio waves.
  - (f) What happens to the overall gain in positive feedback when  $A\beta = 1$  ?
  - (g) What is comparator ?
  - (h) Name one application of positive and negative feedback.
  - (i) A 500 W carrier is modulated to depth of 60%. Calculate the total power in the modulated wave.
  - (j) What is pinch off voltage in FET ?  $8 \times \frac{1}{2} = 4$