

(i) Printed Pages : 3

Roll No.

(ii) Questions : 7

Sub. Code :

0	5	4	5
---	---	---	---

Exam. Code :

0	0	0	6
---	---	---	---

B.A./B.Sc. (General) 6th Semester
(2053)

PHYSICS

Paper—B : Electronics and Solid State Devices-II

Time Allowed : Three Hours]

[Maximum Marks : 44

Note :— Attempt five questions in all, including Question No. 7 (Unit-III) which is compulsory and selecting two questions each from Unit I & II. Use of non-programmable calculator is allowed.

UNIT—I

1. (a) Draw the structure of an n-channel depletion type MOSFET. Explain how the depletion region is formed in the channel. Can depletion type MOSFET be operated in enhancement mode ? 6
- (b) A common source FET amplifier uses a load resistance $200\text{ k}\Omega$. If a.c drain resistance and transconductance of FET are $100\text{ k}\Omega$ and 0.15 mA/V respectively. Calculate the magnitude of the voltage gain of the amplifier. 3
2. (a) What is feedback ? Explain how does the gain of the amplifier can be stabilized with the help of negative feedback and also helps in reducing the non-linear distortion 6

- (b) Draw an emitter follower circuit diagram. Justify that it is a common collector amplifier circuit. 3
3. Sketch the circuit of Wein-Bridge oscillator. Explain the principle of its operation and find an expression for the frequency of oscillations. Show that the amplifier used in it must have a gain greater than 3 for sustained oscillations. 9

UNIT—II

4. (a) What is multivibrator? Derive an expression for frequency and duty cycle of astable multivibrator using IC555. 6
- (b) Draw the block diagram of OP-AMP. Write its characteristics. 3
5. (a) Show that when a radio wave enters the ionosphere, its phase velocity is greater than the velocity of light. 6
- (b) The maximum peak to peak voltage of an AM wave is 8mV and minimum peak to peak voltage is 4mV.
- Calculate :
- (i) the percentage modulation
- (ii) the amplitude of the unmodulated carrier wave. 3
6. (a) How do you realize OR gate using NAND gate? Draw its symbol and truth table. 3
- (b) State and prove De Morgan's theorem. 3
- (c) Construct a simplified logic circuit having output
- $$Y = A.B + A.(B + C) + B.(B + C) \quad 3$$

UNIT—III

(Compulsory Question)

7. Attempt any **eight** parts :

- (a) Explain why audio signals are used to modulate a carrier wave for their transmission.
- (b) What do you understand by minterms and maxterms ?
- (c) What do you mean by open loop and closed loop amplification of OP-Amp ?
- (d) Explain the term virtual height in case of sky waves.
- (e) State the condition under which a feedback amplifier works as an oscillator.
- (f) Define common mode rejection ratio.
- (g) What is pinch off voltage ?
- (h) Define transconductance and amplification factor of a FET.
- (i) In ionosphere, why sky wave propagation is generally better at nights than during the day ?
- (j) Convert the following decimal number $(10.625)_{10}$ to binary number.

$$8 \times 1 = 8$$