

(i) Printed Pages : 3

Roll No.

(ii) Questions : 7

Sub. Code :

0	4	4	9
---	---	---	---

Exam. Code :

0	0	0	5
---	---	---	---

B.A./B.Sc. (General) 5th Semester

(2123)

PHYSICS

Paper-B : Electronics & Solid State Devices-I

Time Allowed : Three Hours]

[Maximum Marks : 44

Note :—(1) Attempt *five* questions in all, including Question No. 7 (Unit-III) which is compulsory and selecting *two* questions each from Unit I-II.

(2) Use of non-programmable calculator is allowed.

UNIT—I

1. Discuss the various parts of cathode ray tube along with diagram in detail and explain the importance of aquadag coating. 9
2. (i) State and explain Thevenin's theorem with example. 6
(ii) The reverse saturation current at room temperature (27 °C) of germanium diode is $3\mu\text{A}$. Find the magnitude of the voltage to be applied across the junction to get a forward current of 30 mA. 3

3. (i) Derive an expression for position of fermi level in an intrinsic semiconductor and how does its position change when acceptor atoms are being added to it ? 6
- (ii) Explain principle, construction and working of a LED. Write its applications and uses. 3

UNIT—II

4. (i) Draw a circuit diagram for full wave rectifier with C-filter and explain its working. Discuss its ripple factor. 6
- (ii) Explain the working of bridge rectifier. 3
5. (i) Define stability and stability factor. Explain the factors responsible for the shift of operating point of the transistor and define transistor biasing. 6
- (ii) A transistor with common base having $\alpha = 0.98$ gives reverse saturation current $I_{CBO} = 10\mu A$ when used in CE mode. It gives the base current of 0.1 mA. Calculate total collector current in CE mode. 3
6. What are the three transistor configurations ? Explain the input and output characteristics of common base transistor circuit. 9

UNIT—III

7. Attempt any *eight* :—

- (i) What is time base circuit ? 1
- (ii) What is a voltage multiplier circuit ? 1

- (iii) What is the h-parameters in the circuit ? 1
- (iv) Why does half-wave rectifier have lower efficiency than full-wave rectifier ? 1
- (v) Define thermal run-away. 1
- (vi) Explain the need of doping in the transistor. 1
- (vii) Explain a good rectifier should have a low ripple factor. 1
- (viii) Define reverse saturation current. 1
- (ix) Define peak inverse voltage (PIV). 1
- (x) Transistor is a current controlled device. Explain. 1